

AIM: Design 8 Bit ALU using Verilog/VHDL.

Software: Iverilog, GTKWAVE, Quartus Prime, Modelsim.

Pin Description:

Pin Names	Description
A0 - A7	Operand Input (ACTIVE HIGH)
B0 - B7	Operand Input (ACTIVE HIGH)
S0 - S2	Function Select Inputs (ACTIVE HIGH)
M	Mode Control Input
C_in/Cn	Carry Input
FO - F7	Function Outputs (ACTIVE HIGH)
Cout	Carry Output

Function Table :

Mode Select Inputs			ACTIVE HIGH OUTPUTS	
S2	S1	S0	LOGIC (M = 0)	ARITHMETIC (M = 1)
0	0	0	A & B	A plus B plus cn
0	0	1	A B	A minus B minus cn
0	1	0	A ^ B	A + 1
0	1	1	~(A B)	B + 1
1	0	0	A << 2	A - 1
1	0	1	B << 2	B - 1
1	1	0	A >> 2	A
1	1	1	B >> 2	B

Procedure:

1. In following ALU, I had used the three bit Control Line to select the operation of ALU and to select the mode there is separate pin M which is active High.
2. For Example: for M : 1 (Arithmetic Mode) Control Word: 010, Then ALU will perform Increment A.
3. In Verilog Code I have used simple case statements for different functions of ALU.
4. And Implemented same verilog Code in **Hardware(on CYCLONE2 FPGA)**

Verilog Code:

```
//Verilog Code for 8 bit ALU.
//Omkar Bhilare, 191060901

module ALU( A, B, c_in, control_line, mode_select, out, c_out);

input [7:0] A, B;          //8 Bit input A and B
input c_in;                //C in input
input [2:0] control_line;  //3 Bit control line for selecting ALU
                             operation
input mode_select;          //Mode = 1 = ARITHMETIC :: Mode = 0 =
                             LOGICAL

output reg c_out;           //C out output for arithmetic
output reg [7:0] out;       //8 Bit output reg

always@(*)
begin
    if(mode_select)
    begin
        case(control_line)
            3'd0 : {c_out, out} = A + B + c_in;
            3'd1 : {c_out, out} = A - B - c_in;
            3'd2 : {c_out, out} = A + 1'b1;
            3'd3 : {c_out, out} = B + 1'b1;
            3'd4 : {c_out, out} = A - 1'b1;
            3'd5 : {c_out, out} = B - 1'b1;
            3'd6 : begin out = A; c_out = 0; end
            3'd7 : begin out = B; c_out = 0; end
            default: out = 8'd0;
        endcase
    end
end
```

```

        endcase
    end
    else
    begin
        c_out = 0;          //Keeping C out LOW in Logical Mode
        case(control_line)
            3'd0 : out = A & B;
            3'd1 : out = A | B;
            3'd2 : out = A ^ B;
            3'd3 : out = ~ (A | B);
            3'd4 : out = A << 2;
            3'd5 : out = B << 2;
            3'd6 : out = A >> 2;
            3'd7 : out = B >> 2;
            default: out = 8'd0;
        endcase
    end
end
endmodule

```

TestBench Code:

```

//Test Bench for ALU
`include "ALU.v"

module ALU_TB();

    reg [7:0] a, b;
    reg C_IN;
    reg [2:0] CONTROL_LINE;
    reg MODE_SELECT;

    wire [7:0]OUT;
    wire C_OUT;
    integer i;
    integer j;
    //Creating ALU instant

```

```

ALU i1
(
    .A(a),
    .B(b),
    .c_in(C_IN),
    .control_line(CONTROL_LINE),
    .mode_select(MODE_SELECT),
    .out(OUT),
    .c_out(C_OUT)
);

initial
begin
    $monitor($time, "  a = %b b = %b cin = %b ::  out = %b  cout = %b
    :: mode = %b control_word = %b", a, b, C_IN, OUT, C_OUT, MODE_SELECT,
CONTROL_LINE);
    //$dumpfile("a.vcd");
    //$dumpvars(0, ALU_TB);
end

initial
begin
    a = 8'd2; b = 8'd3; C_IN = 0;
    MODE_SELECT = 0;
    CONTROL_LINE = 3'd0;
    for(i = 0; i < 2; i++)
    begin
        #5 MODE_SELECT = i; CONTROL_LINE = 3'd0;
        for(j = 1; j < 8; j++)
            #5 CONTROL_LINE = j;
    end
    #5 $finish;
end
endmodule

```

Output:

- **Hardware Implementation on Cyclone 2 FPGA:**


A = 07h

B = 03h

ALU mode = 1 (Arithmetic)

ALU control signal = 000 (ADD)


Output = 0Ah

 


- **Compilation Output:**

Total Logic Cells Used: 99

(of ALTERA CYCLONE2)

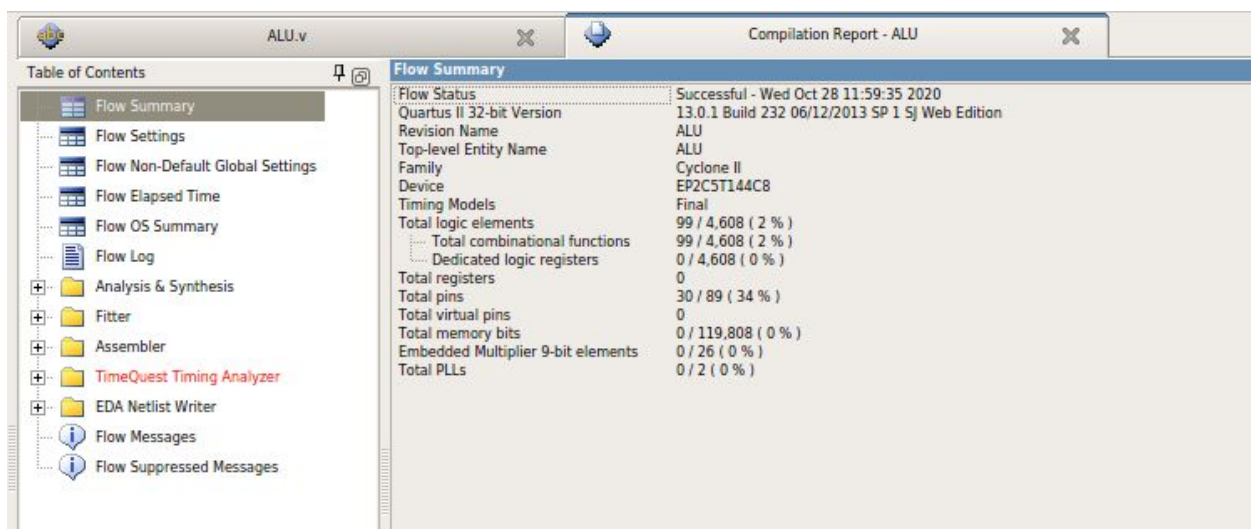

- **GTKWAVE output:**

 

In Above output, control word is varying from 000 to 111 for mode select 0(**Logical Operation**), then once again changing from 000 to 111 for mode select 1 (**Arithmetic Operation**)

Operands: **A: 02 :: B: 03 :: c_in = 0**

For Mode Select 0: Logical Operation

1. Control Word (000h) : A & B: 00000010 & 00000011 = 0000 0010 (**02h**)
2. Control Word (001h) : A | B: 00000010 | 00000011 = 0000 0011 (**03h**)
3. Control Word (010h) : A ^ B: 00000010 ^ 00000011 = 0000 0001 (**01h**)
4. Control Word (011h) : ~(A | B): ~(00000010 | 00000011) = 1111 1100 (**FCh**)
5. Control Word (100h) : A << 2: 00000010 left shift by 2 = 0000 1000 (**08h**)
6. Control Word (101h) : B << 2: 00000011 left shift by 2 = 0000 1100 (**0Ch**)
7. Control Word (110h) : A >> 2: 00000010 right shift by 2 = 0000 0000 (**00h**)
8. Control Word (111h) : B >> 2: 00000011 right shift by 2 = 0000 0000 (**00h**)

For Mode Select 1: Arithmetic Operation

9. Control Word (000h) : A + B: 00000010 + 00000011 = 0000 0101 (**05h**)
10. Control Word (001h) : A - B: 00000010 - 00000011 = 1111 1111 (**FFh**) {-1}
11. Control Word (010h) : A + 1: 00000010 + 1 = 0000 0011 (**03h**)
12. Control Word (011h) : B + 1: 00000010 + 1 = 0000 0100 (**04h**)
13. Control Word (100h) : A - 1: 00000010 - 1 = 0000 0001 (**01h**)
14. Control Word (101h) : B - 1: 00000011 - 1 = 0000 0010 (**02h**)
15. Control Word (110h) : A : 00000010 = 0000 0010 (**02h**)
16. Control Word (111h) : B: 00000011 = 0000 0011 (**03h**)

CONCLUSION:

Thus, I have implemented 8 Bit ALU code using verilog and tested the code in software with different operations in GTKWAVE and as well in quartus prime and finally I have implemented 8 BIT ALU verilog code in Altera Cyclone 2 FPGA