

**AIM:** Design 8 Bit ALU using Verilog/VHDL.

**Software:** Iverilog, GTKWAVE, Quartus Prime, Modelsim.

**Pin Description:**

Pin Names	Description
<b>A0 - A7</b>	Operand Input ( <b>ACTIVE HIGH</b> )
<b>B0 - B7</b>	Operand Input ( <b>ACTIVE HIGH</b> )
<b>S0 - S2</b>	Function Select Inputs ( <b>ACTIVE HIGH</b> )
<b>M</b>	Mode Control Input
<b>C<sub>in</sub>/C<sub>n</sub></b>	Carry Input
<b>FO - F7</b>	Function Outputs ( <b>ACTIVE HIGH</b> )
<b>Cout</b>	Carry Output

**Function Table :**

Mode Select Inputs			ACTIVE HIGH OUTPUTS	
<b>S2</b>	<b>S1</b>	<b>S0</b>	<b>LOGIC (M = 0)</b>	<b>ARITHMETIC (M = 1)</b>
0	0	0	A & B	A plus B plus cn
0	0	1	A   B	A minus B minus cn
0	1	0	A ^ B	A + 1
0	1	1	~(A   B)	B + 1
1	0	0	A << 2	A - 1
1	0	1	B << 2	B - 1
1	1	0	A >> 2	A
1	1	1	B >> 2	B

### Procedure:

1. In following ALU, I had used the three bit Control Line to select the operation of ALU and to select the mode there is separate pin M which is active High.
2. For Example: for M : 1 (Arithmetic Mode) Control Word: 010, Then ALU will perform Increment A.
3. In Verilog Code I have used simple case statements for different functions of ALU.
4. And Implemented same verilog Code in **Hardware(on CYCLONE2 FPGA)**

### Verilog Code:

```
//Verilog Code for 8 bit ALU.
//Omkar Bhilare, 191060901

module ALU( A, B, c_in, control_line, mode_select, out, c_out);

input [7:0] A, B;          //8 Bit input A and B
input c_in;                //C in input
input [2:0] control_line;  //3 Bit control line for selecting ALU
                             operation
input mode_select;          //Mode = 1 = ARITHMETIC :: Mode = 0 =
                             LOGICAL

output reg c_out;           //C out output for arithmetic
output reg [7:0] out;       //8 Bit output reg

always@(*)
begin
    if(mode_select)
    begin
        case(control_line)
            3'd0 : {c_out, out} = A + B + c_in;
            3'd1 : {c_out, out} = A - B - c_in;
            3'd2 : {c_out, out} = A + 1'b1;
            3'd3 : {c_out, out} = B + 1'b1;
            3'd4 : {c_out, out} = A - 1'b1;
            3'd5 : {c_out, out} = B - 1'b1;
            3'd6 : begin out = A; c_out = 0; end
            3'd7 : begin out = B; c_out = 0; end
            default: out = 8'd0;
        endcase
    end
end
```

```

        endcase
    end
    else
    begin
        c_out = 0;          //Keeping C out LOW in Logical Mode
        case(control_line)
            3'd0 : out = A & B;
            3'd1 : out = A | B;
            3'd2 : out = A ^ B;
            3'd3 : out = ~ (A | B);
            3'd4 : out = A << 2;
            3'd5 : out = B << 2;
            3'd6 : out = A >> 2;
            3'd7 : out = B >> 2;
            default: out = 8'd0;
        endcase
    end
end
endmodule

```

#### TestBench Code:

```

//Test Bench for ALU
`include "ALU.v"

module ALU_TB();

    reg [7:0] a, b;
    reg C_IN;
    reg [2:0] CONTROL_LINE;
    reg MODE_SELECT;

    wire [7:0]OUT;
    wire C_OUT;
    integer i;
    integer j;
    //Creating ALU instant

```

```

ALU i1
(
    .A(a),
    .B(b),
    .c_in(C_IN),
    .control_line(CONTROL_LINE),
    .mode_select(MODE_SELECT),
    .out(OUT),
    .c_out(C_OUT)
);

initial
begin
    $monitor($time, "  a = %b b = %b cin = %b ::  out = %b  cout = %b
    :: mode = %b control_word = %b", a, b, C_IN, OUT, C_OUT, MODE_SELECT,
CONTROL_LINE);
    //$dumpfile("a.vcd");
    //$dumpvars(0, ALU_TB);
end

initial
begin
    a = 8'd2; b = 8'd3; C_IN = 0;
    MODE_SELECT = 0;
    CONTROL_LINE = 3'd0;
    for(i = 0; i < 2; i++)
    begin
        #5 MODE_SELECT = i; CONTROL_LINE = 3'd0;
        for(j = 1; j < 8; j++)
            #5 CONTROL_LINE = j;
    end
    #5 $finish;
end
endmodule

```

**Output:**

- **Hardware Implementation on Cyclone 2 FPGA:**


**A = 07h**

**B = 03h**

**ALU mode = 1 (Arithmetic)**

**ALU control signal = 000 (ADD)**

**Output = 0Ah**

 

- **Compilation Output:**


**Total Logic Cells Used: 99**

**(of ALTERA CYCLONE2)**

Table of Contents	
Flow Summary	
Flow Settings	
Flow Non-Default Global Settings	
Flow Elapsed Time	
Flow OS Summary	
Flow Log	
Analysis & Synthesis	
Filter	
Assembler	
TimeQuest Timing Analyzer	
EDA Netlist Writer	
Flow Messages	
Flow Suppressed Messages	

Flow Summary	
Flow Status	Successful - Wed Oct 28 11:59:35 2020
Quartus II 32-bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Web Edition
Revision Name	ALU
Top-level Entity Name	ALU
Family	Cyclone II
Device	EP2C5T144C8
Timing Models	Final
Total logic elements	99 / 4,608 ( 2 % )
Total combinational functions	99 / 4,608 ( 2 % )
Dedicated logic registers	0 / 4,608 ( 0 % )
Total registers	0
Total pins	30 / 89 ( 34 % )
Total virtual pins	0
Total memory bits	0 / 119,808 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 26 ( 0 % )
Total PLLs	0 / 2 ( 0 % )

- **GTKWAVE output:**

 

In Above output, control word is varying from 000 to 111 for mode select 0(**Logical Operation**), then once again changing from 000 to 111 for mode select 1 (**Arithmetic Operation**)

Operands:    **A: 02        ::        B: 03        ::        c\_in = 0**

### **For Mode Select 0: Logical Operation**

1. Control Word (000h) : A & B: 00000010 & 00000011    = 0000 0010 (**02h**)
2. Control Word (001h) : A | B: 00000010 | 00000011    = 0000 0011 (**03h**)
3. Control Word (010h) : A ^ B: 00000010 ^ 00000011    = 0000 0001 (**01h**)
4. Control Word (011h) : ~(A | B): ~(00000010 | 00000011)    = 1111 1100 (**FCh**)
5. Control Word (100h) : A << 2: 00000010 left shift by 2    = 0000 1000 (**08h**)
6. Control Word (101h) : B << 2: 00000011 left shift by 2    = 0000 1100 (**0Ch**)
7. Control Word (110h) : A >> 2: 00000010 right shift by 2    = 0000 0000 (**00h**)
8. Control Word (111h) : B >> 2: 00000011 right shift by 2    = 0000 0000 (**00h**)

### **For Mode Select 1: Arithmetic Operation**

9. Control Word (000h) : A + B: 00000010 + 00000011    = 0000 0101 (**05h**)
10. Control Word (001h) : A - B: 00000010 - 00000011    = 1111 1111 (**FFh**) {-1}
11. Control Word (010h) : A + 1: 00000010 + 1                = 0000 0011 (**03h**)
12. Control Word (011h) : B + 1: 00000010 + 1                = 0000 0100 (**04h**)
13. Control Word (100h) : A - 1: 00000010 - 1                = 0000 0001 (**01h**)
14. Control Word (101h) : B - 1: 00000011 - 1                = 0000 0010 (**02h**)
15. Control Word (110h) : A :        00000010                = 0000 0010 (**02h**)
16. Control Word (111h) : B:        00000011                = 0000 0011 (**03h**)

## **CONCLUSION:**

Thus, I have implemented 8 Bit ALU code using verilog and tested the code in software with different operations in GTKWAVE and as well in quartus prime and finally I have implemented 8 BIT ALU verilog code in Altera Cyclone 2 FPGA